

## 2018-2019 Term 2

### PHYS1001 Essential Physics


#### Assignment 7

Due date: 26<sup>th</sup> March, 2019 by 6:00 pm

(Please leave your homework in the box with the label “PHYS 1001” outside room 213 in Science Centre North Block)

Please answer all five questions

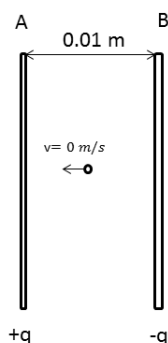1. An electron, originally placed at the mid-point between the two charged planes, starts from rest. It is known that the electric field between the two plates is uniform and has a value of 0.002 N/C. Ignore the effect of gravitation in the calculation. Given that the mass of an electron is  $9.11 \times 10^{-31}$  kg.



- (a) Calculate the electric force on the electron.  
(b) Calculate the time it takes the electron to reach plate A.

Answer:

(a)

$$\begin{aligned} F &= qE \\ F &= (1.6 \times 10^{-19})(0.002) \\ F &= 3.2 \times 10^{-22} \text{ N} \end{aligned}$$

(b)

$$\begin{aligned} F_{\text{net}} &= ma \\ 3.2 \times 10^{-22} &= (9.11 \times 10^{-31})a \\ a &= 0.351 \times 10^9 \text{ m/s}^2 \\ s &= \frac{0.01}{2}, u = 0, a = 0.351 \times 10^9, t = ? \\ s &= ut + \frac{1}{2}at^2 \\ \frac{0.01}{2} &= \frac{1}{2}(0.351 \times 10^9)t^2 \\ t &= 5.34 \times 10^{-6} \text{ s} \end{aligned}$$


2. A student measures the resistance of an unknown resistor experimentally by collecting the potential difference  $V$  across the resistor and the current passing through the resistor.

$V/\text{volts}$	2	4	6	8	10	12
$I/\text{mA}$	16	32	49	63	80	96

- (a) Plot a graph of  $V$  against  $I$ . Label your graph properly.  
 (b) What is the meaning of the slope of the graph? Find the value of the slope.

Answer:


(a)

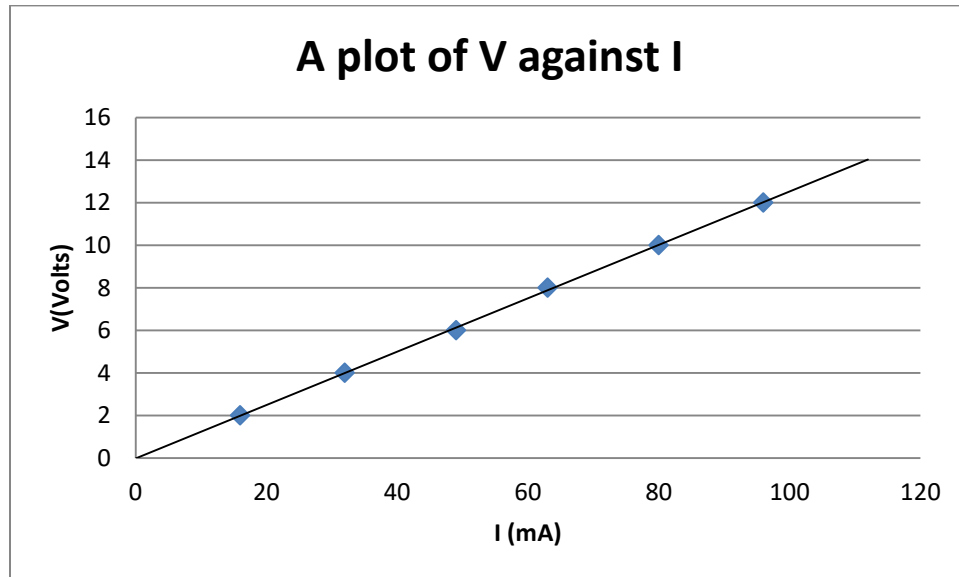

- (b) The slope is the resistance of the resistor.


$$R = \frac{12 - 2}{(96 - 16) \times 10^{-3}} = 125 \, \Omega$$

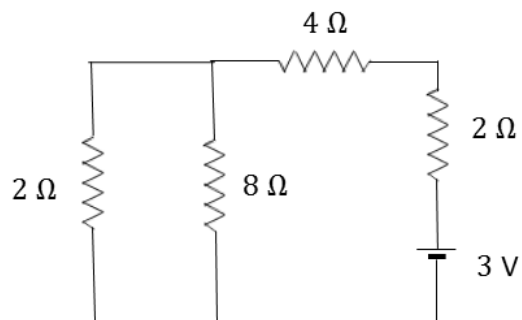3. (a) Calculate the current passing through each resistor.




- (b) Calculate the power consumed by each resistor.

Answer:

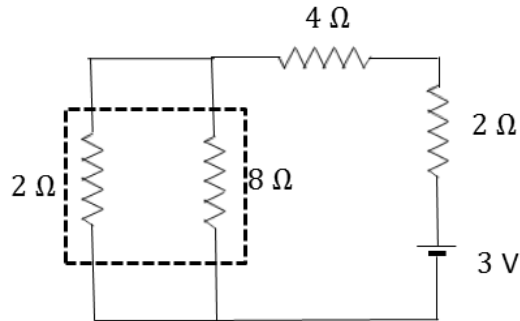


$$\frac{1}{\text{Equivalent resistance}} = \frac{1}{2} + \frac{1}{8}$$
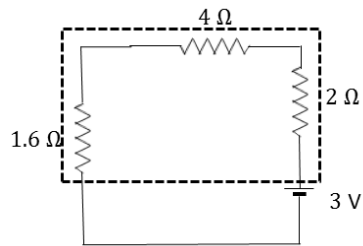
$$\text{Equivalent resistance} = 1.6 \Omega$$


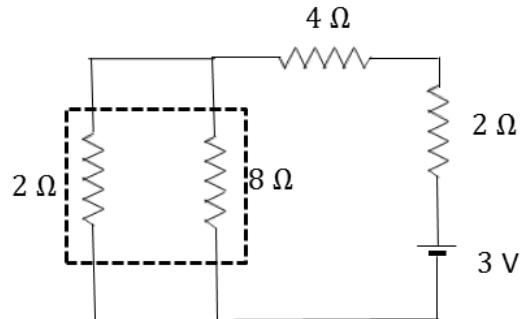
$$\text{Equivalent resistance} = 1.6 + 4 + 2 = 7.6 \Omega$$



$$\text{Current passing through the } 2 \Omega \text{ and } 4 \Omega \text{ resistor} = \frac{3}{7.6} = 0.395 \text{ A}$$

$$\text{Potential difference across the } 8 \Omega \text{ resistor} = 3 - 2 \times 0.395 - 4 \times 0.395 = 0.63 \text{ V}$$

$$\text{Current passing through the } 2 \Omega \text{ resistor} = 0.316 \text{ A}$$

$$\text{Current passing through the } 8 \Omega \text{ resistor} = 0.080 \text{ A}$$


$$\text{(b) Power of the } 2 \Omega \text{ resistor (the } 2 \Omega \text{ resistor in parallel with the } 8 \Omega \text{ resistor)} = I^2 R = (0.316)^2 (2) = 0.2 \text{ W}$$

$$\text{Power of the } 8 \Omega \text{ resistor} = I^2 R = (0.08)^2 (8) = 0.05 \text{ W}$$

$$\text{Power of the } 4 \Omega \text{ resistor} = I^2 R = (0.395)^2 (4) = 0.62 \text{ W}$$

$$\text{Power of the } 2 \Omega \text{ resistor (the } 2 \Omega \text{ resistor in the rightmost branch)} = I^2 R = (0.395)^2 (2) = 0.31 \text{ W}$$

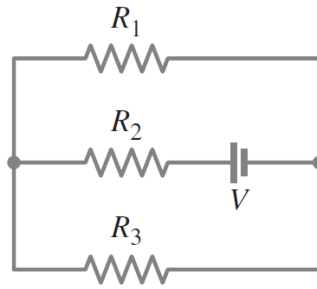4. In the circuit below, the resistance of resistors 1, 2 and 3 are  $10\ \Omega$ ,  $5\ \Omega$  and  $10\ \Omega$  respectively. The EMF of the battery is  $5\text{V}$ .



- (a) Calculate the current passing through  $R_2$ .  
 (b) Calculate the voltage across  $R_1$  and  $R_3$

Answer:

- (a)  $R_1$  and  $R_3$  are connected in parallel

$$\frac{1}{R_1} + \frac{1}{R_3} = \frac{1}{R_{eq}}$$

$$R_{eq,A} = 5\ \Omega$$

$R_{eq,A}$  and  $R_2$  are connected in series

$$R_{eq,total} = 5 + 5 = 10\ \Omega$$

The current passing through  $R_{eq,total}$  is:

$$V = IR_{eq,total}$$

$$I = \frac{V}{R_{eq,total}}$$

$$I = \frac{5}{10}$$

$$I = 0.5\ \text{A}$$

- (b) The potential difference across  $R_2$  is  $V = IR_2 = (0.5)(5) = 2.5\ \text{V}$

The potential difference across  $R_1$ :


$$V_1 = -V_2 + \text{E. M. F.}$$

$$V_1 = 5 - 2.5$$

$$V_1 = 2.5\ \text{V}$$

Similarly, the potential difference across  $R_3$  is also  $2.5\ \text{V}$ .

5. Consider the following circuit:

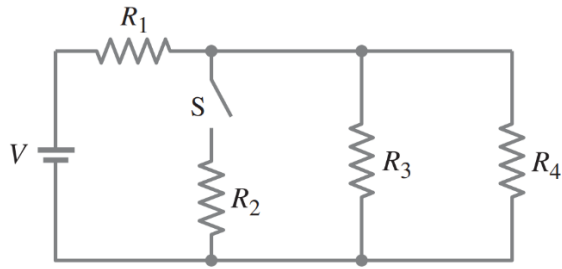

The resistance of each resistor is  $10\ \Omega$  and  $V = 100\text{ V}$ .

- Before the switch is closed, calculate the currents through each resistor.
- After the switch is closed, calculate the currents through each resistor.

Answer:

- Before the switch is closed,  $R_3$  and  $R_4$  are connected in parallel.

$$\frac{1}{R_3} + \frac{1}{R_4} = \frac{1}{R_{eq,A}}$$

$$R_{eq,A} = 5\ \Omega$$

$R_{eq,A}$  is connected in series with  $R_1$ .

$$R_{eq,total} = 5 + 10 = 15\ \Omega$$

The current through the battery:

$$V = IR_{eq,total}$$

$$100 = I(15)$$

$$I = 6.67\text{ A}$$

The current through  $R_1$  is 6.67 A. The current passing through  $R_3$  is  $\frac{6.67}{2} = 3.33\text{ A}$ . Similarly, the current passing through  $R_4$  is  $\frac{6.67}{2} = 3.33\text{ A}$ .

- After the switch is closed,  $R_2$ ,  $R_3$  and  $R_4$  are connected in parallel.

$$\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} = \frac{1}{R_{eq,A}}$$

$$R_{eq,A} = 3.33\ \Omega$$

$R_{eq,A}$  is connected in series with  $R_1$ .

$$R_{eq,total} = 3.33 + 10 = 13.33\ \Omega$$

The current through the battery:

$$V = IR_{eq,total}$$

$$100 = I(13.33)$$

$$I = 7.5 \text{ A}$$

The current through  $R_1$  is 7.5 A. The current passing through  $R_2$  is  $\frac{7.5}{3} = 2.5$  A. Similarly, the current through each resistor  $R_3$  and  $R_4$  is  $\frac{7.5}{3} = 2.5$  A